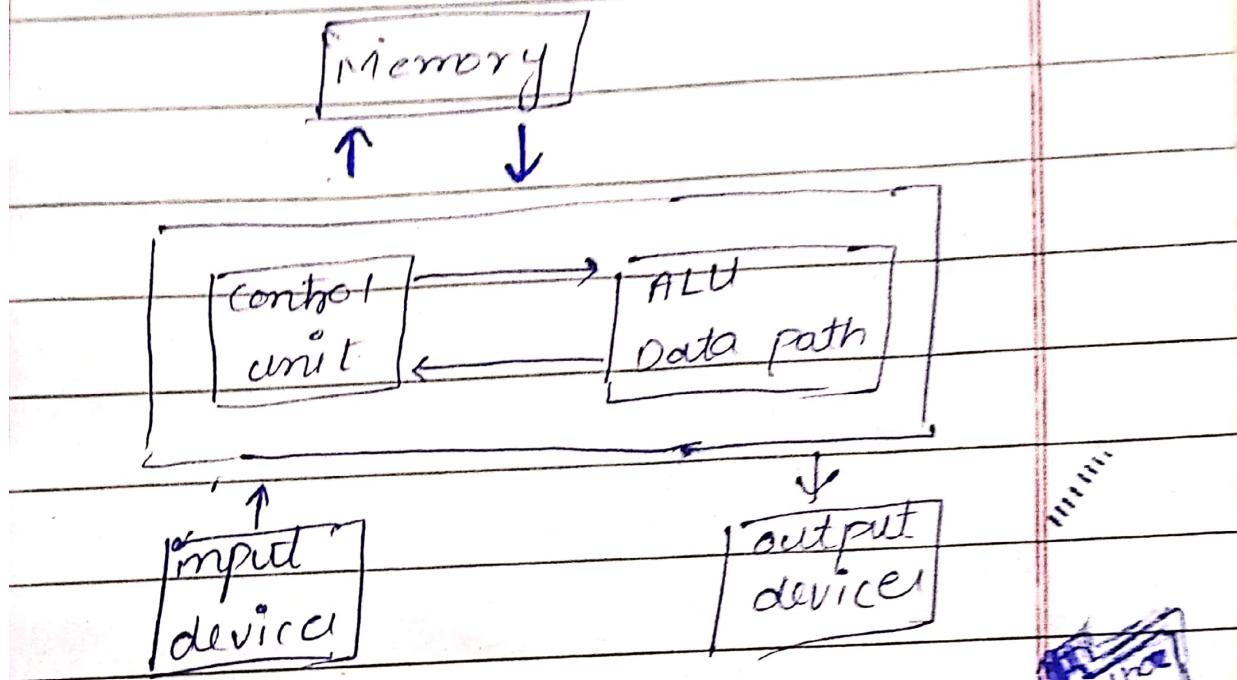


Block diagram of digital computer:



- Arrows shows flow of data.
- Different components of computer system are shown in diagram.
- memory save data and programs.

* What are different input devices?

* Which are different output devices?

Data path:

Arithmetic and logic

control unit : controls everything

e.g.:

Flow of program.

Running the system.

Running program fetching
code line one by one.

Sample program:

integer a, b, c

input a;

input b ;

c = a + b

print c;

→ if you are a control units-

• How control unit running the



sample program .

• Data is travelling from
one to other component

- Data coming from keyboard.
- Addition in data path.
- storing in memory.
- Display on screen LCD.

How is data travelling?

Data travels in the form of signals.

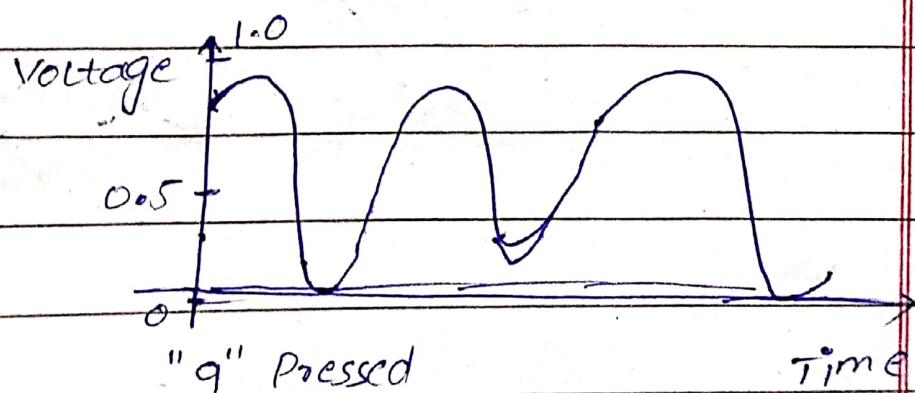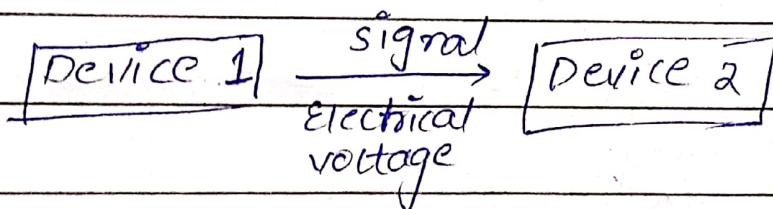


Keyboard → signal → CPU


How will we save signal as "q"?

For this we define a range of voltage.


input signal

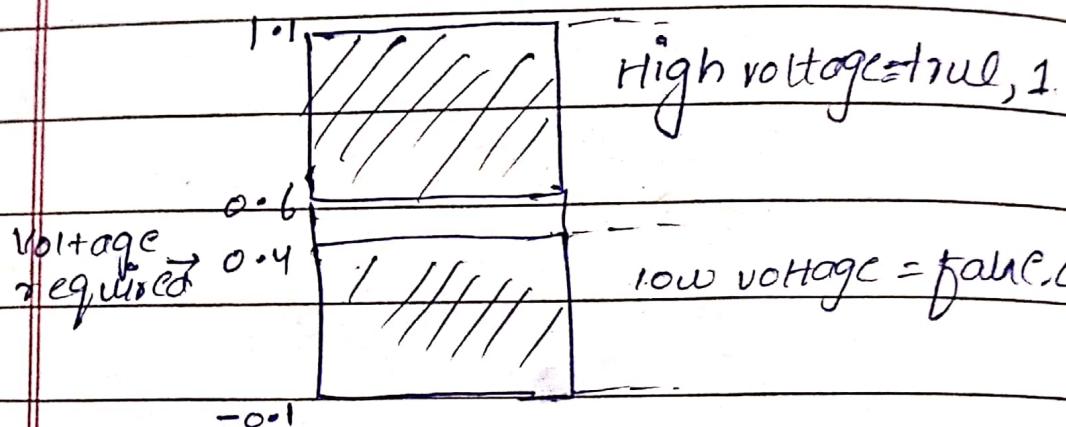

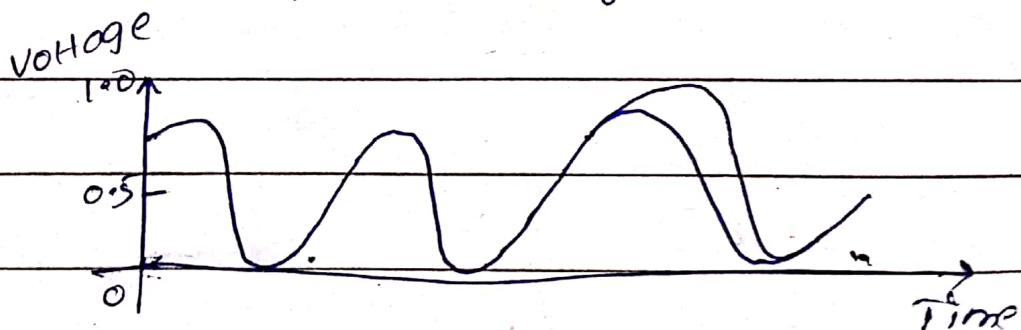Now voltage has been converted to 0/1 binary number.



voltage

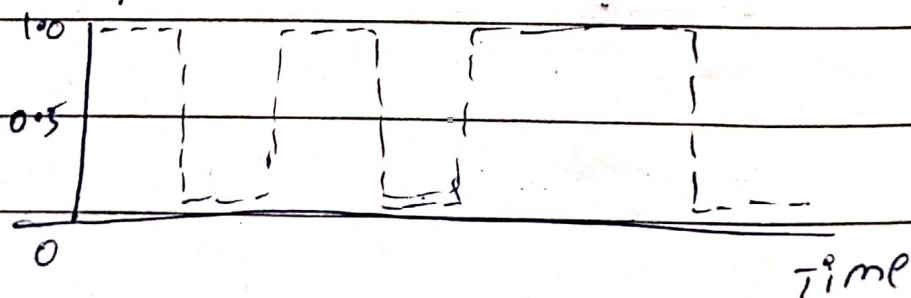

if dotted line indicate start of a binary number which

Binary numbers have we received
in above signal?

Answer: ? 1010110

This is now data is sent/received
from/to a device.

This 0/1 is called binary
digit or bit.

↳ Binary to decimal conversion?

$$(11010)_2 = (?)_{10}$$

$$1 \times 2^4 + 1 \times 2^3 + 0 \times 2^2 + 1 \times 2^1 + 0 \times 2^0 \\ 16 + 8 + 0 + 2 + 0$$

$$= (26)_{10}$$

As it is $\frac{1}{2}^{-ve}$ powerⁿ.

$$(11010.11)_2 = (?)_{10}$$

$$2^6 + 1 \times 2^{-1} + 1 \times 2^{-2}$$

$$2^6 + 0.5 + 0.25$$

$$(26.75)_{10}$$

Decimal to binary?

$$(0.25)_{10} = (?)_2$$

2	625
2	312 - 1
2	156 - 0
2	78 - 0
2	39 - 0
2	19 - 1
2	9 - 1
2	4 - 1
2	2 - 0
	1 - 0

$$(1001110001)_2$$

→ fraction form:

as → integer fraction
is ↑ ↑

$$(625 \cdot 6875)_{10} = (?)_2$$

Multiply fraction part by 2:

$$\cdot 6875 \times 2 = 1 \cdot 3750 \quad 1$$

$$\cdot 3750 \times 2 = 0 \cdot 7500 \quad 0$$

$$\cdot 7500 \times 2 = 0 \cdot 5000 \quad 1$$

$$\cdot 5000 \times 2 = 1 \cdot 000 \quad 1$$

$$(0 \cdot 6875)_{10} = (0 \cdot 1011)_2$$

→ separate both parts

→ convert integer part as it is.

→ convert fraction part as above.

Repeat process until

fraction becomes 0.0000 OR

sufficient accuracy obtained

$$(0 \cdot 6875)_{10} = (0 \cdot 1011)_2$$

$$(625 \cdot 6875)_{10} = (1001110001 \cdot 1011)_2$$

Type:

We have 4 types of number systems.

1. Decimal (Base - 10)
2. Binary (Base - 2)
3. Octal (Base - 8)
4. Hexadecimal (Base - 16)

We have seen decimal number system representations.

We can represent
 $(724 \cdot 542)_{10}$ Most significant → least significant

$$(7 \times 10^2 + 2 \times 10^1 + 4 \times 10^0 + 5 \times 10^{-1} + 4 \times 10^{-2}) + 2 \times 10^{-3}$$

$$9871 \quad 9870$$

newly
changed (8)871

Digits in base - 10 number system are

$$0, 1, 2, 3, \dots, 9$$

i.e

Digits in base - α

$$0, 1, 2, \dots, \alpha - 1$$

where α is base

or radix.

why A, B, C include in hexadecim al?

Ans: To differentiate it from decimal

$$C15_{16} = (?)_{10}$$

$$1 \times 16^1 + 5 \times 16^0 = \dots$$

↳ when 1 and 5 are different numbers

F

$$15 \times 16^0 = ??$$

when ^{it is} ~~decimal~~ F

Lecture 2

Data Ranges:

Let me represent

1 bit with one box



→ Minimum value it can have $\boxed{0}$


→ Maximum value it can

have $\boxed{1}$

Range $0 \rightarrow 1$

the 8 digit number
in decimal
 $\begin{array}{cccccc} & & & & & \\ \text{x} & \text{x} & \text{x} & \text{x} & \text{x} & \text{x} \\ \text{0} & \text{0} & \text{0} & \text{0} & \text{0} & \text{0} \\ \text{9} & \text{9} & \text{9} & \text{9} & \text{9} & \text{9} \end{array}$

if we have 2 bits

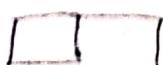

Min value it can have $\boxed{00}$

Max value it can have $\boxed{11}$

All possible value of 2 bits

Range of value $0 \rightarrow 3$

00	0
01	1

formula

11	2
----	---

$$0 \rightarrow 2^n - 1$$

$1, 2, 4, 8, 16, 32, 64, 128$

$$2^0, 2^1, 2^2, 2^3, 2^4, 2^5, 2^6$$

Range of fractions:

$$0 \rightarrow \frac{2^n - 1}{2^n}$$

Conventions:

Normally we say $10^3 \rightarrow \text{kilo}$

$$\begin{aligned} 4 \text{ kg} &= 4 \times 10^3 \text{ g} \\ &= 4 \times 1000 \text{ g} \\ &= 4000 \text{ g} \end{aligned}$$

but in dealing with data

$$2^{10} = 1024$$

$$2^{10} = \text{kilo (K)}$$

$$1 \text{ KB} = 1024 \text{ byte}$$

$$2^{20} = \text{Mega (M)}$$

$$16 \text{ M} = 16 \times 2^{20} \text{ byte}$$

$$2^{30} = \text{Giga (G)}$$

$$2^{40} = \text{Tera (T)}$$

{ Arithmetic operations }

Addition:

Decimal addition revision

if Ans > Base

\downarrow
to add →

765

498

1259

(10)¹⁵
,012

M T W T F S

H/W □ C/W □

DATE: 1 / 120

Binary number:

 $\frac{2}{1} \overline{)20}$

10

Ex 1 01100

 $\frac{213}{117}$

10001

11101

Ex 2: 10110

2+1

10111

10

101101

Hexadecimal addition:

A 10

$$\begin{array}{r}
 & 16 | 19 \\
 & \underline{- 1 - 3} \\
 59F & \\
 + E46 & \swarrow \text{spare} \\
 \hline
 1B E5
 \end{array}$$

B 11
C 12
D 13
E 14
F 15

$$\begin{array}{r}
 \overset{10}{\cancel{7}} \overset{10}{\cancel{5}} \\
 \overset{10}{\cancel{4}} \overset{10}{\cancel{6}} \\
 \hline
 16 | 21 \\
 \underline{- 1 - 5} \\
 \hline
 1 \text{ and } 3
 \end{array}$$

Binary subtraction:

$$\begin{array}{r}
 10110 \\
 - 10010 \\
 \hline
 00100
 \end{array}$$

M T W T F S

H/W C/W 7051
1923
1041

DATE: 1/120

Ex 2:

$$\begin{array}{r}
 10.1\overset{+2}{1}0\overset{+2}{2} \text{ decimal} \\
 - 10011\overset{-19}{1} \\
 \hline
 0.0011\overset{3}{3}
 \end{array}$$

~~10~~~~10~~

if upper value is smaller than
lower than replace values.

and write " $-^u$ " minus with it

$$\begin{array}{r}
 10011\overset{-19}{1} \\
 - 11110\overset{-30}{0}
 \end{array}$$

~~1010~~
~~| |
|----|
| 10 |
| 5 |
| 2 |
| 2 |
| 1 |
| 0 |~~

10011 < 11110

$$\begin{array}{r}
 100110 \\
 - 111105 \\
 \hline
 10101 \\
 - 10101 \\
 \hline
 13 \\
 - 13 \\
 \hline
 0
 \end{array}$$

~~19+5~~~~1611105~~~~1~~ ~~F~~~~19~~~~10101~~~~E~~ ~~4~~ ~~6~~~~15+6=21~~~~13~~ ~~E~~ ~~5~~~~16+3~~~~3 E3~~~~16+3~~

Octal Multiplications

$$\begin{array}{r} 162 \\ \times 15 \\ \hline 760 \\ 120 \\ \hline 242 \end{array}$$

$$136 \times 10 = 1360$$

$$\begin{array}{r} 240 \\ \times 8 \\ \hline 1920 \end{array}$$

$$762 \times 15$$

$$\begin{array}{r} 102 \\ \times 27 \\ \hline 510 \\ 204 \\ \hline 276 \end{array}$$

$$\begin{array}{r} 4672 \\ \times 3700 \\ \hline 13772 \end{array}$$

$$8 \sqrt{170} \quad 8 \mid 170$$

$$10 \sqrt{100} \quad 10 \mid 100$$

↳ Binary to octal / Hexadecimal
conversion:

Consider following binary.

(1011000110101111000001)₂
→ 25 digits

Binary → Base n - conversion

For base $= 2^n$, we need minimum n bits to represent any digit of that base

$$\text{Base } 8 = 2^3$$

This method is valid for 2^n only.

For octal we represent number

Octal	Binary	Binary	In 3 bits
0	000	0	we cannot
1	001	01	represent
2	010	10	all octal
3	011	11	digit in in 1 or 2 bits.
4	100	100	
5	101	101	
6	110	110	
7	111	111	

consider a decimal number

0000 7890 5260 000 → no change

$$(010 \cdot 110 \ 0010110 \ 1011110000)$$

$$\begin{array}{r} 011 \\ \times 2 \end{array}$$

$$\begin{array}{r} 10110 \\ \times 2 \\ \hline 00110 \end{array}$$

$$\begin{array}{r} 10110 \\ \times 2 \\ \hline 00110 \end{array}$$

$$\begin{array}{r} 00110 \\ \times 2 \\ \hline 00110 \end{array}$$

$$\begin{array}{r} 10011 \\ \times 2 \\ \hline 11110 \end{array}$$

SHOW

$$(673 - 12)_8 = (?)_2$$

$$(3A6 - C)_{16} = (?)_2$$

$$(E59C - 04B)_{16} = (?)_8 \quad 11110$$

ANSWER

Binary coding decimal (0.1010ϕ)

$$\begin{array}{r} 10110 \\ - 10010 \\ \hline 00100 \end{array} \quad \begin{array}{r} 10110 \\ - 10010 \\ \hline 00100 \end{array}$$

Lecture #3

Binary coded decimal:

Decimal	Binary
0	0000
1	0001
2	0010
3	0011
4	0100
5	0101
6	0110
7	0111
8	1000
9	1001

largest no is 9

So we need 4 bits for it.

This conversion is called

binary coded decimal (BCD)
conversion.

→ Decimal to BCD:

$$(396)_{10} = (?)_{BCD}$$

every digit is taken individually.

$$\begin{array}{cccc} 0 & 0 & 1 & 1 \\ 1 & 0 & 0 & 1 \\ 0 & 1 & 1 & 0 & 1 \end{array} \quad \text{BCD}$$

$$(X)_{BCD} \neq (X)_2$$

$$(396)_{10} = (?)_2$$

$$(396)_{10} = (110001100)_2 \neq (001110010110)_2 \quad \text{BCP}$$

$$\begin{array}{r}
 396 \\
 \hline
 2 | 198 \\
 2 | 99 \\
 2 | 49 \\
 2 | 24 \\
 2 | 12 \\
 2 | 6 \\
 2 | 3 \\
 2 | 1
 \end{array}$$

BCD to decimal:

(00011 0000101)_{BCD}

(185)₁₀

Binary Number

Signed Binary number

unsigned binary number

signed magnitude representation

a's complement representation

① Unsigned numbers

$n-1 \ n-2$



2 1 0

\Rightarrow Range

← magnitude →

only

$0 \rightarrow 2^n - 1$

example: 4 bit no

$0 \rightarrow 2^4 - 1$

Range: 0000

.....

Bit Extension:

e.g. making 6 bit number
from original

4 bit no:

e.g. 976

make it 6 digit

000976

$$(9)_{10} = (1001)_2$$

make 8 bit no:

$$(9)_{10} = (00001001)_2 \text{ F } (1001)_2$$

(2) Signed numbers

sign Representation

+ → 0

- → 1

we need to represent "+" and "-" sign in binary form 0/1 for n-bit numbers



$0 \rightarrow +$ Total $n-1$ bits

$1 \rightarrow -$ to save magnitude

Range

For example 4 bit no:

- +ve no Range → sign mag

0 000 + 0

+ 0

0 111 + 7

- -ve no Range → 1000 - 0

+ 0

1 111 - 7

Bit extension:- 4 bit to 8 bit

$$(+9)_{10} = (01001)_2$$

↓

$$(00001001)_2$$

$$= (+9)_{10}$$

$$(-9)_{10} = (11001)_2$$

$$= (10001001)_2$$

$$= (-9)_{10}$$

For n-bit numbers:-

$$-(2^{n-1}-1) + 0 + (2^{n-1}-1)$$

NOTE:-

The left most bit
represents sign.

signed
decimal

magnitude
representation in sign
magnitude

+7	0111	0111
+6	0110	0110
+5	0101	0101
+4	0100	0100
+3	0011	0011
+2	0010	0010
+1	0001	0001
+0	0000	0000
-0	1000	0000
-1	1001	1111
-2	1010	1110
-3	1011	1101
-4	1100	1100
-5	1101	1011
-6	1110	1010
-7	1111	1001
-8	(11000)	1000

cannot be represented
in 4 bits.

Signed 2's complement
representation:

2's complement of No-(Algorithm)


$$N = 10100100$$

1. Start traversing bits from right to left.
2. Leave or copy all data as it is until
3. Copy 1st 1. 7st 7 coms.
4. Flip rest of bits i.e. 0-01, 1-00. module module

2's complement of $N = 0101100$

* positive nos are identical in both representations.

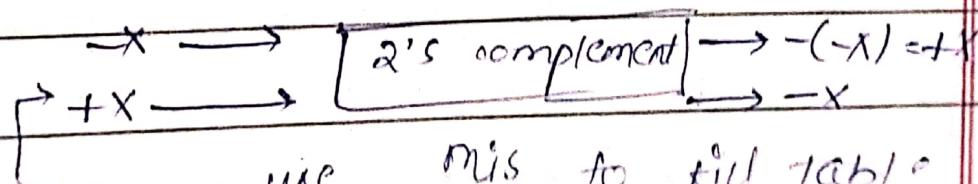
* In both systems left most bit represents sign.



use this to fill table

Signed 2's complement &
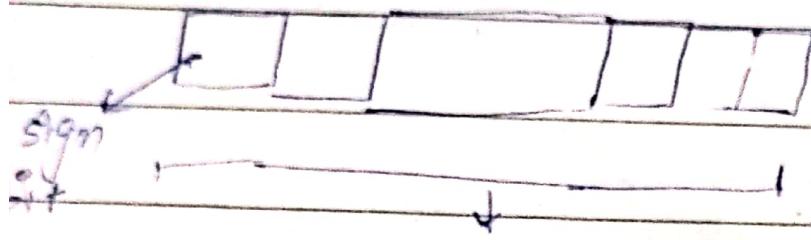
$$n-1 \quad n-2 \quad \dots \quad 2 \quad 1 \quad 0$$



magnitude bit n total n bits

available for magnitude

2's complement

magnitude

Range:

e.g. 4 bit no sig neg

+ve nos Range: $(0000)_2 \rightarrow (10)_10$

$(0111)_2 \rightarrow (7)_10$

-ve numb Range:

$1000_2 \rightarrow 1111_2$
2's complement
 $\rightarrow -1000_2 \quad ?(0001)_2$

$(-8)_10 \quad (-1)_10$

Range $E - (2^{n-1})_2 \rightarrow 0 + 2^n - 1$

BH extension:

DATE: 1/120

What is this no in 2's complement representation.

$$(0111)_2 = 7$$

4 + 0 8 bit

$$(00000111)_2$$

Lecture 4

Formula to find 2's complement:

$$2^n - N$$

N is any binary number

Algorithms of subtraction:

1. Borrows Method

2. Subtraction using 2's complement

$$(\pm A) - (+B) = (\pm A) + (-B)$$

$$(\pm A) - (-B) = (\pm A) + (+B)$$

Actual operation
performed is addition.
taking 2's complement
before that if necessary.

Reason: In our processor
we do not have separate
hardware for subtraction. We
will use addition hardware.

lessen hardware
sim process

Example:

$$6 - 13 = ?$$

Subtraction using 2's complement
we need to do

$$6 + (-13) \rightarrow$$

• Actually addition
will be performed

Step 1:

unsigned representation

$$6 = 110$$

$$13 = 1101$$

Step 2:

signed representation

$$+6 = 0110$$

$$+13 = 01101$$

Step 3:

Bit extension

$$+6 = 00110$$

$$+13 = 001101$$

Step 4:

Make no of bits same

$$+6 = 000\ 110$$

$$+13 = 001\ 101$$

Step 5:

$$A - B = A + (-B)$$

$$+6 = 000\ 110 \quad 2's$$

$$+(-13) = 110011 \quad \text{com}$$

$$\underline{011001}$$

We are done here let's check 2's com

- 7

and Example:

$$-6 - 13 = ?$$

we need to do $-6 + (-13)$

Step 1 unsigned Rep

$$6 = 110$$

$$13 = 1101$$

Step 2 signed Rep

$$+6 = 0110$$

$$+13 = 01101$$

Step 3 Bit Extension

$$+6 = 00110$$

$$+13 = 001101$$

Step 4 Make no of bits same

$$+6 = 000110$$

$$+13 = 001101$$

Step 5 $-A - B = -A + (-B)$

* Why we do bit extension?

we have same number
of bits - 8 available in three
numbers A, B, C.

$$C = A + B$$

For example without bit extension

$$-8 - 8 = -8 + (-8)$$

$$\begin{array}{r} \text{discard} \\ -8 \end{array} \quad \begin{array}{r} 1000 \\ \hline 0000 \end{array}$$

$$1000$$

$$\underline{0000} \rightarrow \text{wrong ans}$$

↳ with bit extension

$$-8 = \begin{array}{l} \text{disc} \\ \text{out} \end{array} 11000$$

$$-8 = \begin{array}{r} 11000 \\ \hline 0000 \end{array}$$

$$\underline{0000} \rightarrow \text{correct ans}$$

$$= \begin{array}{r} \checkmark \\ -16 \end{array}$$

* Why we discard last carry?

e.g. $m-n = 13-6 = ?$

M T W T F S

H/W □ - C/W □

DATE: 1 / 1 / 20

$$\begin{array}{r} M = 13 \\ N = 6 \end{array} \rightarrow \begin{array}{r} 1101 \\ 0110 \end{array} \quad \begin{array}{r} 1101 \\ 00110 \end{array}$$

$$\begin{array}{r} M - N \\ 11010 \\ \hline \text{discard } 00011 \end{array}$$

$$8\text{'s comp of } N = 2^3 - N$$

$$M - N$$

$$\begin{aligned} & M + 2^3 \text{ comp of } N \\ &= M + (2^3 - N) \\ &= M - N + \cancel{(2^3)} \\ &\quad \checkmark \quad \downarrow \text{discard} \end{aligned}$$

$$\begin{array}{r} 000111 \\ + 100000 \\ \hline + 7 \end{array}$$

Hardware components that manipulate binary info is called "Digital Circuit".


→ Digital circuit are performing different operations.

→ Basic circuit is called logic

Gate → base of all circuit

Multiple logic gate make complex circuit.

(one or more)

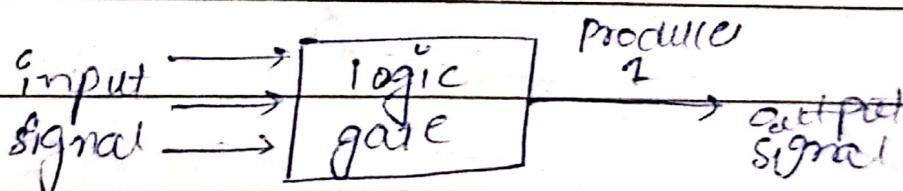

outputs of gate are applied to inputs of other gates to form digital circuit.

(Electrical signal i.e voltage/current exist throughout a digit system in either of two recognizable values)

→ Each gate performs a specific logical operation.

Three basic logic operations associated with binary variable.

- AND
- OR
- NOT

→ AND Gate:

perform AND operation.


operation Representation

$$Z = X \cdot Y$$

or Read as Z is

$Z = XY$ equal to 'X and Y'

Graphical symbol:

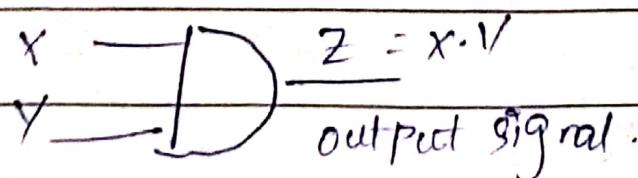

input
signal

Truth Table

INPUT		OUTPUT
X	Y	Z
0	0	0
0	1	0
1	0	0
1	1	1


Truth table: Table showing all possible inputs and their corresponding outputs.

↳ OR Gate:

perform OR operation

$$Z = X + Y$$

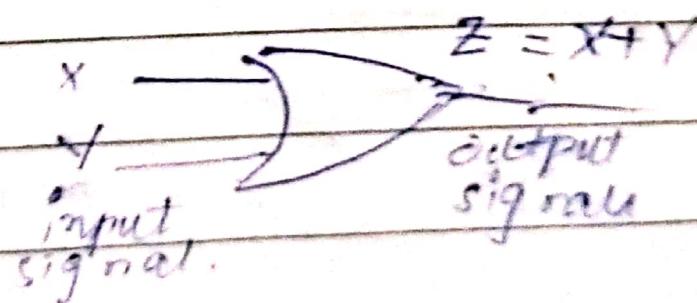Read as Z is equal to X OR Y
graphic symbol?



Truth table:

X	Y	$Z = X + Y$
0	0	0
0	1	1
1	0	1
1	1	1

↳ NOT Gate:

- performs complement operation.


- operation: Representation:

$$Z = \bar{X} \text{ or } X'$$

Read as Z is equal to

NOT X

- Graphical symbol:

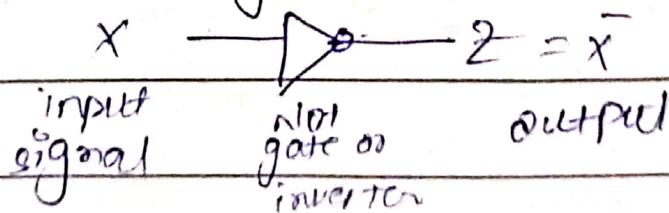

- Truth table:

X	$Z = \bar{X}$
0	1

→ Timing diagram of AND, OR, NOT






Timing diagram:

Signal with
a periodic
voltage

0 or 1

Time

Transitions
(Change in
voltage)

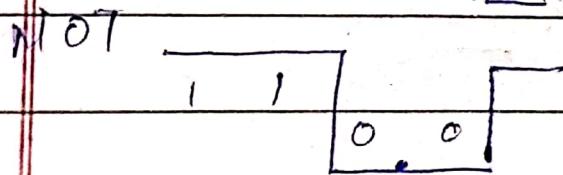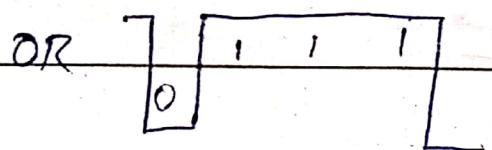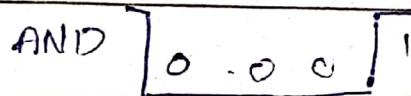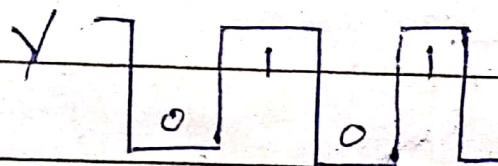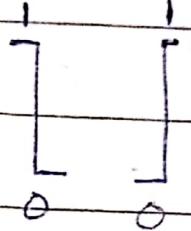

Gate delay:





→ Property of a gate.

The length of time it takes


for an input change to result
in corresponding output change.

- Denoted by L_g
depends on can be different
(for diff.)
 - * Gate type.
 - * No of inputs
 - * underlying technology.
 - * circuit design of gate.


e.g. :

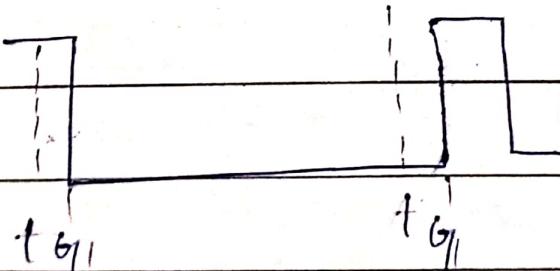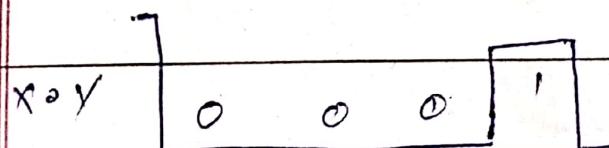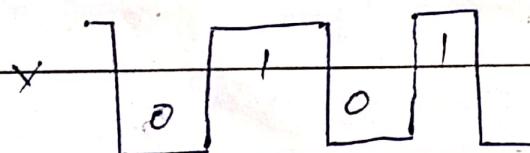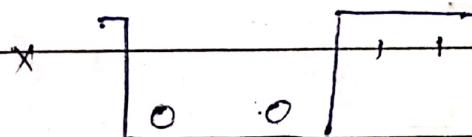

Multiple inputs in gates:

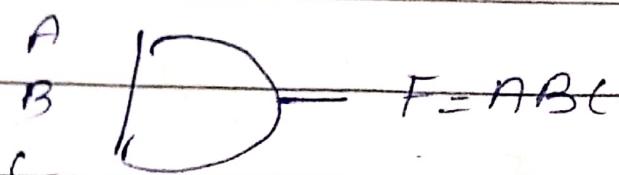

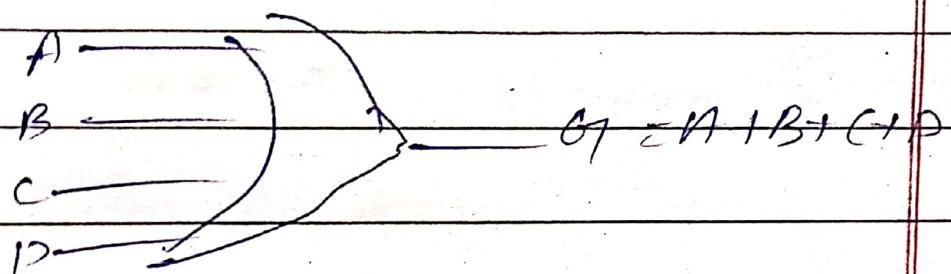
F_1 will be one $(A, B, C) = (1, 1, 1)$
and 0 otherwise (for rest
of comb.)



G_1 will be zero only
when $(A, B, C, D) = (0, 0, 0, 0)$

for rest of combination

G_1 will be 1

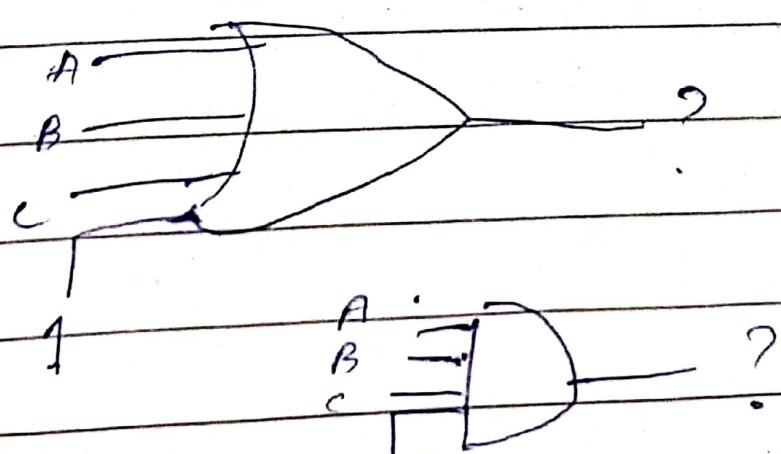

Lecture no 5

→ for n inputs - 2^n

example:

Rows in truth table

$$L = D\bar{X} + A \quad \rightarrow \text{First draw circuit.}$$

$$D \quad X \quad A \quad \bar{X} \quad D\bar{X} \quad L = D\bar{X} + A$$

$$0 \quad 0 \quad 0 \quad 1 \quad 0 \quad 0$$

$$0 \quad 0 \quad 1 \quad 1 \quad 0 \quad 1$$

$$0 \quad 1 \quad 0 \quad 0 \quad 0 \quad 0$$


$$0 \quad 1 \quad 1 \quad 0 \quad 0 \quad 1$$

$$1 \quad 0 \quad 0 \quad 1 \quad 1 \quad 1$$

$$1 \quad 0 \quad 1 \quad 1 \quad 1 \quad 1$$

$$1 \quad 1 \quad 0 \quad 0 \quad 0 \quad 0$$
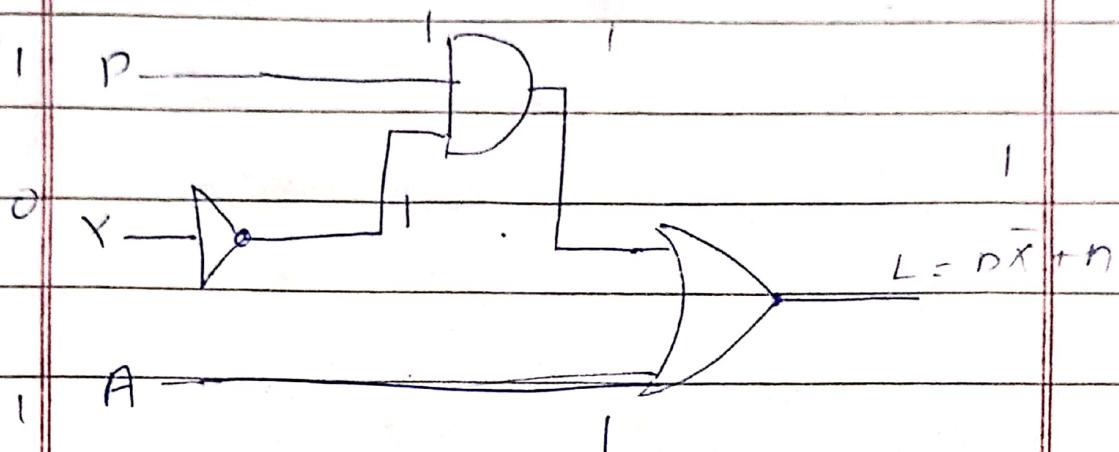
$$1 \quad 1 \quad 1 \quad 0 \quad 0 \quad 1$$



variable are contained with logical operations so these circuits are called combinational logic circuits.

→ Draw the circuit of following function.

- Boolean Algebra:

$$Z = X \cdot X$$

$$Z = \overline{X} \cdot \overline{X}$$

input

- Binary variables: Y, V. 0/1

- Basic logic operations: AND, OR, NOT

$$F = \bar{x} \vee z + x \vee z + x \cdot z$$

M T W T F S

H/W C/W

DATE: ___ / ___ / 20___

term → part of expression

$$Y = \overbrace{DX}^{\text{term}} + A$$

← boolean expression

→ single variable within
term is called literal.

→ we use few identities to simplify Boolean functions.

Basic identities of Boolean algebra.

$$1. \quad x + 0 = x$$

$$2. \quad x \cdot 1 = x$$

$$3. \quad x + 1 = 1$$

$$4. \quad x \cdot 0 = 0$$

$$5. \quad x + x = x$$

$$6. \quad x \cdot x = x$$

$$7. \quad x + \bar{x} = 1$$

$$8. \quad x \cdot \bar{x} = 0$$

$$9. \quad \bar{\bar{x}} = x$$

Both of these columns are dual of each other..

Dual of an equation:

AND → OR
OR → AND

① Interchange AND and OR

② Replace 1's by 0's and 0's by 1's.

equation (1, 3, 5, 7) are

dual of (2, 4, 6, 8)

→ Duality principle: Boolean equation remains valid if we take the dual of expression on both

~~size of equal sign = true.~~

Basic identities of Boolean algebra:

* Commutative law:

i.e

$$10. X + Y = Y + X \quad 11. XY = YX$$

* Associative law:

i.e

$$12. X + (Y + Z) = (X + Y) + Z$$

$$13. X(YZ) = (XY)Z.$$

* Distributive law:

$$14. X(Y + Z) = XY + XZ$$

$$15. X + YZ = (X + Y)(X + Z)$$

* De Morgan's Law:

$$16. \overline{X+Y} = \bar{X} \cdot \bar{Y}$$

$$17. \overline{X \cdot Y} = \bar{X} + \bar{Y}$$

→ proof of distributive law:

start proving from logic

expression.

$$R \cdot H = S = (X+Y)(X+Z) \Rightarrow X \cdot X + X \cdot Y + X \cdot Z + Y \cdot Z$$

$$\because X \cdot X = X \quad X + XZ + XY + YZ \Rightarrow X(1+Z) + XY + YZ$$

$$\therefore 1+Z=1 \quad X + XY + YZ \Rightarrow X(H(Y) + YZ) \Rightarrow X(YZ)$$


Demorgan's theorem with n variables

$$\overline{X_1 + X_2 + \dots + X_n} = \overline{X_1} \cdot \overline{X_2} \cdot \overline{X_3} \cdot \dots \cdot \overline{X_n}$$

$$\overline{X_1 \cdot X_2 \cdot \dots \cdot X_n} = \overline{X_1} + \overline{X_2} + \overline{X_3} + \dots + \overline{X_n}$$

Reduce following function
and draw circuit.
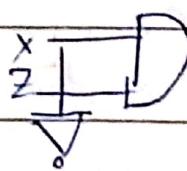
$$\begin{aligned} F &= \overline{XYZ} + \overline{XY\bar{Z}} + XZ \\ &= \overline{X}(YZ + Y\bar{Z}) + XZ \\ &= \overline{X}Y(Z + \bar{Z}) + XZ \\ &= \overline{X}Y(1) + XZ \\ &= \overline{X}Y + XZ \end{aligned}$$





HOMEWORK

Page 9

$$(A+B)(A+CD) = A+BCD$$

→ Consensus theorem

$$XY + \bar{X} \cdot Z + YZ = XY + \bar{X}Z$$

Start from longer side

L.H.S

$$XY + \bar{X}Z + YZ \cdot 1 \quad | \overbrace{\text{---}}^{\text{---} X \cdot 1 = X}$$

$$= XY + \bar{X}Z + YZ (X + \bar{X}) \quad | \overbrace{\text{---}}^{\text{---} X + \bar{X} = 1}$$

$$= XY + \bar{X}Z + XYZ + \bar{X}YZ$$

$$= XY + XYZ + \bar{X}Z + \bar{X}YZ$$

$$= XY(1+Z) + \bar{X}Z(1+Y)$$

$$= XY + \bar{X}Z \quad | \overbrace{\text{---}}^{\text{---} 1+Z = 1}$$

$$= R.O.F.I.S \quad | \overbrace{\text{---}}^{\text{---} 1+Y = 1}$$

What is dual of consensus theorem

$$(A+B)(\bar{A}+C) = AC + B$$

→ complement of a function

$$F_1 = \bar{X}Y\bar{Z} + \bar{X}\bar{Y}Z$$

$$\bar{F}_1 = ?$$

$$\begin{aligned}
 \bar{F}_1 &= \overline{\bar{X}Y\bar{Z} + \bar{X}\bar{Y}Z} && \text{By de Morgan's} \\
 &= (\overline{\bar{X}Y\bar{Z}}) \cdot (\overline{\bar{X}\bar{Y}Z}) && \text{law} \\
 &= (\bar{\bar{X}} + \bar{Y} + \bar{Z})(\bar{\bar{X}} + \bar{Y} + Z) \\
 &= (X + \bar{Y} + \bar{Z})(X + Y + \bar{Z})
 \end{aligned}$$

$$F_2 = X(\bar{X}\bar{Z} + YZ) \quad \bar{F}_2 = ?$$

$$\bar{F}_2 =$$

L complementing function using dual:

Step 0: Add parenthesis around terms.

Add dot (.) in AND

Step 1: Take dual of function

Step 2: Complement each term.

\rightarrow	AND \rightarrow OR OR \rightarrow AND $0 \rightarrow 1$ $1 \rightarrow 0$
---------------	--

$$F_1 = \bar{X} \cdot Y \cdot \bar{Z} + \bar{X} \cdot \bar{Y} \cdot Z$$

$$= (\bar{X} \cdot Y \cdot \bar{Z}) + (\bar{X} \cdot \bar{Y} \cdot Z) \quad \text{step 0}$$

$$\text{dual} = (\bar{X} + Y + \bar{Z})(\bar{X} + \bar{Y} + Z) \quad \text{step 1}$$

$$\bar{F}_1 = (X + \bar{Y} + Z)(X + Y + \bar{Z})$$

$$F_2 = X(\bar{Y} \bar{Z} + Y Z)$$

Using deMorgan's theorem, express the functions:

$$F = A \bar{B} \bar{C} + \bar{A} \bar{C} + A B$$

(a) with only OR and complement operations.

⑥ with only AND and complement
and complement operation.

(a) Solution:

more should not be only
AND gate in circuit.

$$\bar{F} = \overline{ABC} + \overline{AC} + AB$$

$$= (\overline{ABC}) \cdot (\overline{A}\overline{C}) \cdot (\overline{AB})$$

$$= (\bar{A} + B + \bar{C}) \cdot (A + C) \cdot (\bar{A} + \bar{B})$$

$$= (\overline{\bar{A} + B + \bar{C}}) + (\overline{A+C}) + (\overline{\bar{A} + \bar{B}})$$

Lecture n 6

↳ standard forms of Boolean expression:

- A boolean function expressed algebraically can be written in a variety of ways.
2 standard forms are

- * sum of products.
- * Product of sums.

- standard forms facilitate the simplification procedure for boolean expressions.

Standard forms contain:

- product term.
- Sum term -

↳ product terms:-


"logical product (AND)

operation of n literals"

e.g:-

$$x\bar{y}z,$$

1 product term

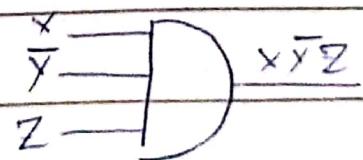


Literals can be complemented or uncomplemented.

↪ Sum term:-

↳ logical sum (OR)
operation of n literals

e.g.: 1 sum term

$$\underline{X + Y + \bar{Z}},$$

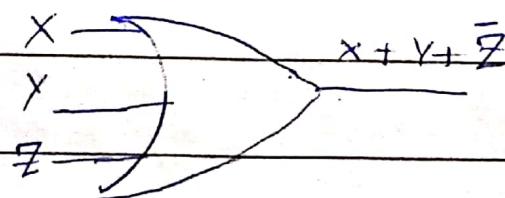

Sum of product forms-


output $\leftarrow F = \underbrace{\text{product term}_1}_{\text{variable}} + \underbrace{\text{product term}_2}_{1} + \underbrace{\text{product term}_3}_{2} + \underbrace{\text{product term}_4}_{3} - \dots + \underbrace{\text{product term}_n}_{n}$

product term_i = product of $1 \rightarrow n$ literals.


e.g.:

$$F = \underbrace{\bar{Y}}_{1 \text{ literal}} + \underbrace{\bar{X}Y\bar{Z}}_{3 \text{ literals}} + \underbrace{XY}_{2 \text{ literals}}$$

Total product term = 3

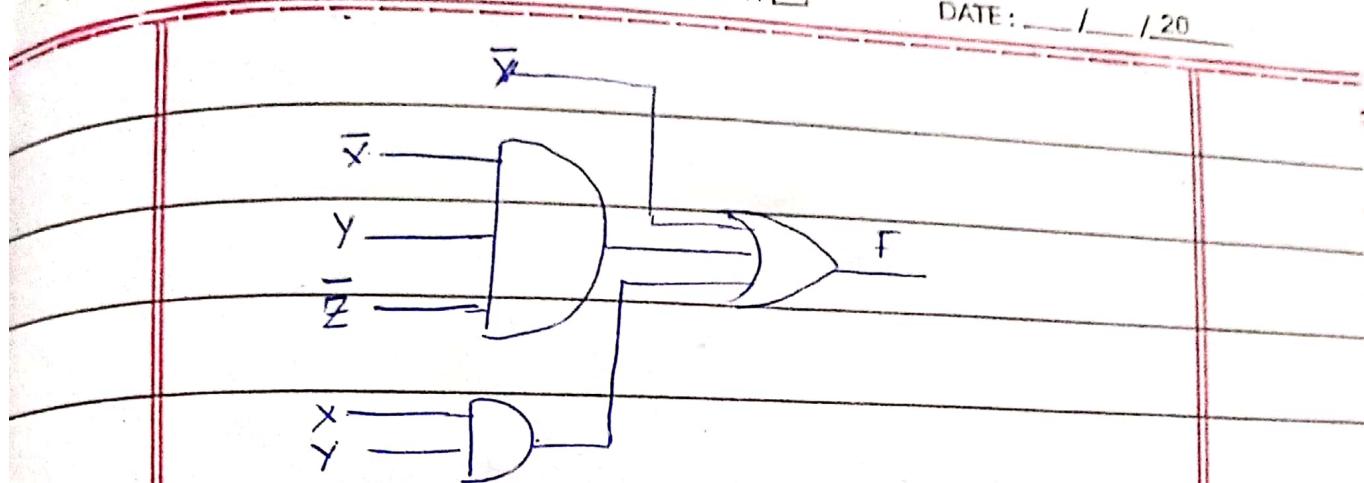

Standard form of sum of product circuit.

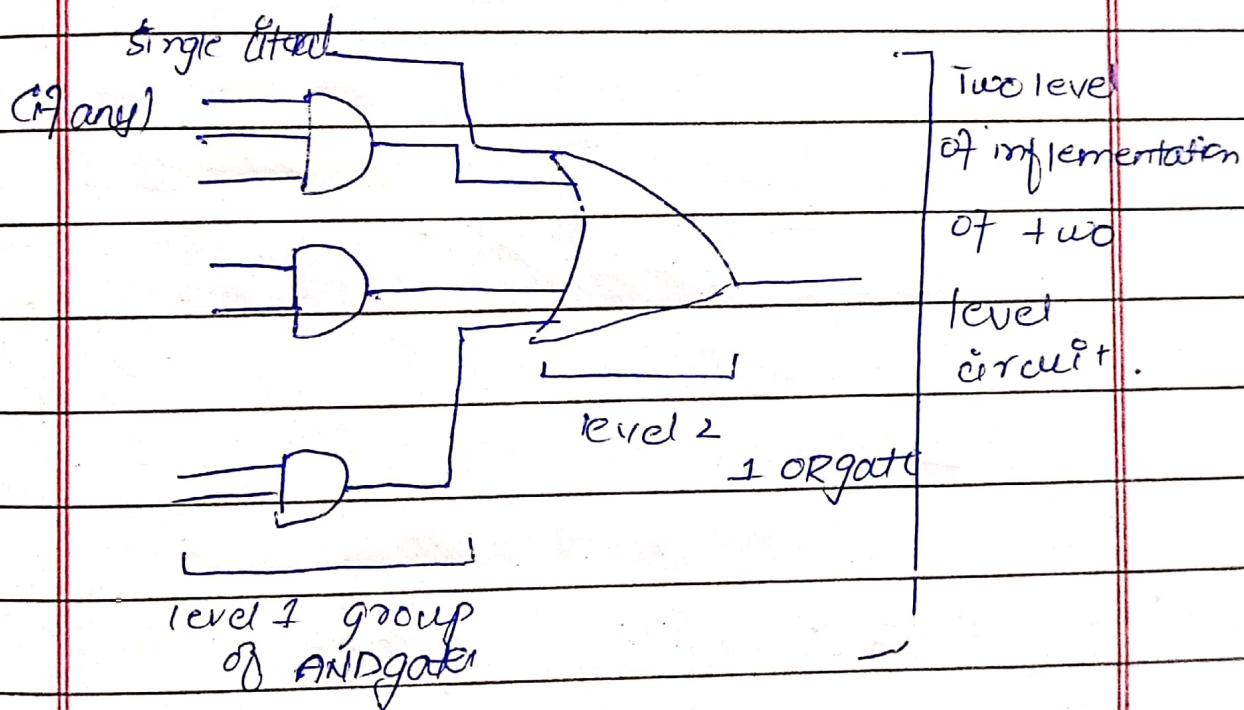

we assume that input variable are directly available in their complemented or uncompimented terms . so inverters are not included in diagram .

Is following function in sum of product form?


$$F = AB + C(D+E)$$

It is not sum of product form.

H should be a

$$F = AB + CD \cdot CE \checkmark$$

$$F = AB + C(D+E)$$

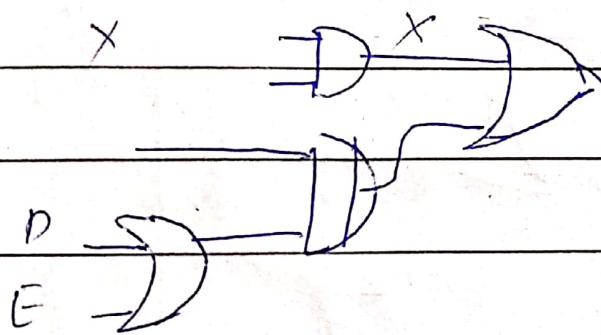

Product of sum terms:

$$F = (\text{sum term}_1) \cdot (\text{sum term}_2) \cdot (\text{sum term}_3) \cdot \dots \cdot (\text{sum term}_n)$$


sum term_i = logical sum of 1-Hom terms

For e.g.:


$$F = X \cdot (\bar{Y} + Z) \cdot (X + Y + \bar{Z})$$

↓ sum terms → ~~term 1~~
 sum term 1 2 - terms sum term 3
 1 - literal 2 - literal 3 - literal

Implementation configuration

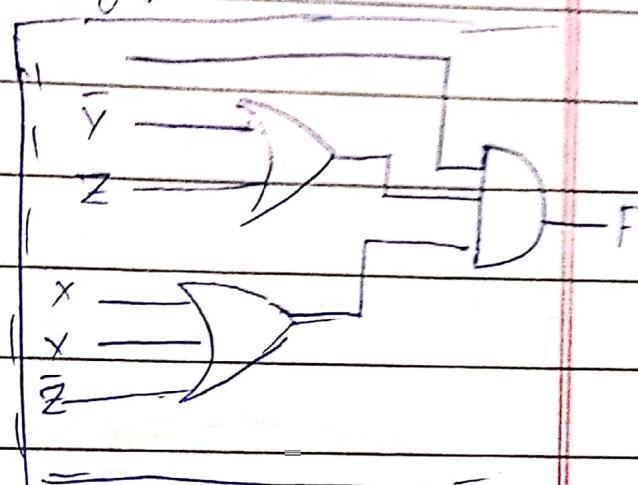

single literal
if any

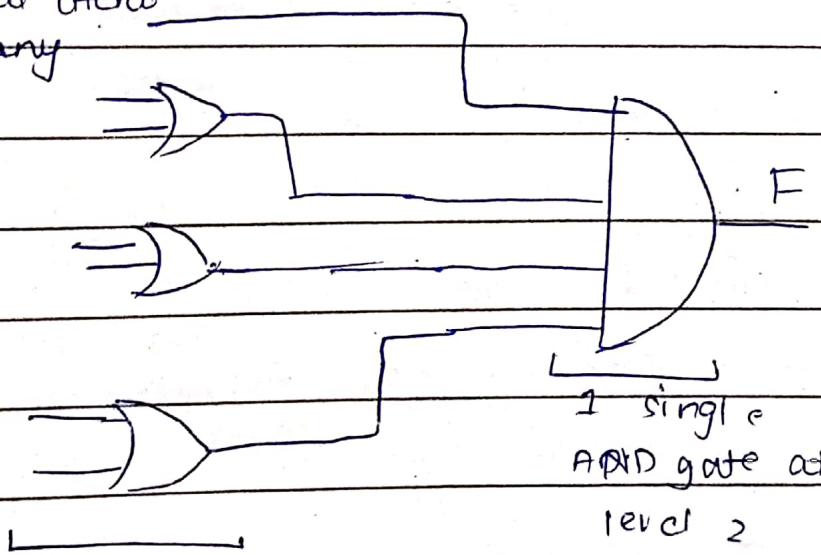

group of OR
gates at level 1

→ single expression results in ⇒ the level of getting structure

Note: if we talk about m, it will be
1 other all are 0.

M T W T F S

H/W □ C/W □

DATE: 1 / 1 / 20

M T Y

Minterms and Maxterms

X, Y, Z Total variables = 3

Total combination = 2^3 For each binary

Basically there are all possible product terms which we can write using X Y Z | Product term → mere product terms are called minterms.

3 variables	0 0 0	$\bar{X} \bar{Y} \bar{Z}$ = 1 on this combination m ₀
-------------	-------	--

0 0 1 $\bar{X} \bar{Y} Z$ For the corresponding m₁

0 1 0 $\bar{X} Y \bar{Z}$ input combination m₂

0 1 1 $\bar{X} Y Z$ gives output 1 m₃

1 0 0 $X \bar{Y} \bar{Z}$ each variable m₄

1 0 1 $X \bar{Y} Z$ includes in each product term m₅

1 1 0 $X Y \bar{Z}$ exactly n m₆

1 1 1 $X Y Z$ variable m₇

Suppose I want to write a product

term in form of XYZ against each combination such that

↳ It includes each variable only one complemented or uncomplemented.

→ Result of Product term is 1 for that combination.

* Minterm and its properties:-

- A product term in which all the variables appear exactly once either complemented or uncomplemented.
- It represents exactly one combination of binary variable value in truth table.
- It has value one for that combination and "0" for all others.

Analysis of tables:-

* For n variable $\rightarrow 2^n$ distinct minterms.

* For $X = 0$ we are writing \bar{x} in minterm.

* " $x = 1$ " " " " x "

Same stands for y and z .

* symbol for each minterm \rightarrow j

$$(j)_{10} = (xyz)_2$$

$$\text{e.g } (0) = (000)_2$$

$$(1) = (001)_2$$

$$(2) = (010)_2$$

Can you write min term for two variables?

Max terms of all variables complemented or uncomplemented.

Write sum term for each combination and it contains

all variables complemented or uncomplemented.

These are called max terms.

X	Y	Z	Sum terms	Symbol	* For each
0	0	0	$X + Y + Z$	m_0	combination containing no terms give result "0".
0	0	1	$X + Y + \bar{Z}$	m_1	
0	1	0	$X + \bar{Y} + Z$	m_2	* includes all variables
0	1	1	$X + \bar{Y} + \bar{Z}$	m_3	exactly one.
1	0	0	$\bar{X} + Y + Z$	m_4	In short therefore
1	0	1	$\bar{X} + Y + \bar{Z}$	m_5	all possible sum terms we can have with
1	1	0	$\bar{X} + \bar{Y} + Z$	m_6	
1	1	1	$\bar{X} + \bar{Y} + \bar{Z}$	m_7	3 variables.

A sum term that contains all the variables in complemented or uncomplemented form.

n variables \Rightarrow 2^n max terms

If $X = 0$ we write X in sum term

" $X = 1$ " " \bar{X} " "

Write possible max terms for 2 variables?

M T W T F S

HW CRM

DATE: 1/120

Lecture 7

(Relation between)

Property

Minterm and Maxterm

$$M_j = \bar{m}_j$$

step 1:

$$\bar{M}_j = m_j$$

write minterms

o.g.:

m_j against each combination

$$m_0 = \bar{x} \bar{y} \bar{z}$$

step 2:

$$\bar{m}_0 = \bar{\bar{x}} \bar{\bar{y}} \bar{\bar{z}}$$

Select combination or

$$= x + y + z$$

minterms which give output.

$$= m_0$$

Step 3: write function
as logical sum of
selected minterms.

Now to derive a function given

8th truth table

XOR	x	y	z	F		F
	0	0	0	1	$\rightarrow \bar{x} \bar{y} \bar{z}$	0
	0	0	1	0	$\oplus \bar{x} y z$	1
	0	1	0	1		0
	0	1	1	0		1
	1	0	0	0	$\rightarrow x \bar{y} z$	0
	1	0	1	0		1
	1	1	0	1	$\rightarrow x y z$	0
	1	1	1	1	$\rightarrow x \bar{y} \bar{z}$	0

Lecture # 8

What is map?

- A diagram made up of squares.
- Each square representing a minterm.

Two-variable map

		x	y	minterms
		0	0	$\bar{x}\bar{y}$
		0	1	$\bar{x}y$
no of variables	= 2 = n			
no of min terms	= $2^2 = 2^n$	1	0	$x\bar{y}$
no of cells/squares	= $2^2 = 2^n$	1	1	xy

0	0	0	$m_0 = 00$	$m_1 = 01$	$m_2 = 10$	$m_3 = 11$
0	1	$\bar{x}y$	$\bar{x}y$	$\bar{x}y$	$x\bar{y}$	xy
1	0	$x\bar{y}$	$x\bar{y}$	$x\bar{y}$	$x\bar{y}$	xy

→ combination

information in cell is only for your learning.

x				
0	0	1		→ no of minima
1	2	3		

How to simplify/optimize
boolean equation using K-map-

Given:

Required simplified
equation

- ① Truth table.
- ② $F(A, B) = \Sigma m(---)$
- ③ Boolean equation

Example:

Two variable K-map

Given:

x	y	F
0	0	1
0	1	1
1	0	0
1	1	1

step 1 :

Draw K-map


step 2 :

check Enter the function
on K-map.

① check the minterms in
the truth table which
are giving value 1

0, 1, 3

② write 1 in those cells.

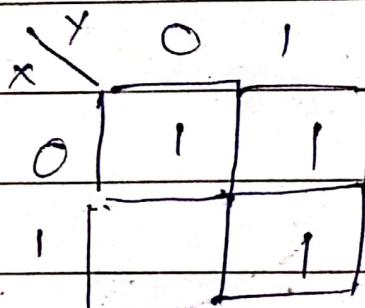

→ Now K-map is showing
information that output
is 1 on minterms
0, 1 and 3


At minterm 2, output

is zero but we don't write
in map as we will be working
on 1s only.

Step 3:

Identify rectangle of
adjacent cells having 1s.

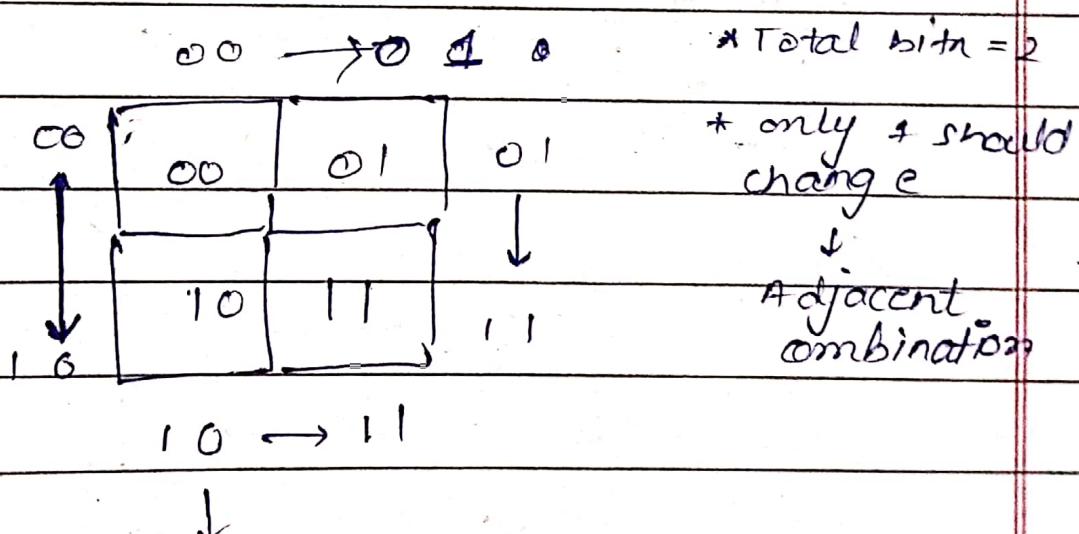* Adjacent cells / combinations →
which differ in value by only 1 bit
& variable.



1 bit changed out of 2 bits

we can define size of rectangle,
as no of 1s in it.

we can make rectangles

of size

2^2 no other

$$2^0 = 1 \quad \boxed{}$$


size allowed

$$2^1 = 2 \quad \boxed{} \quad \boxed{}$$

→ either horizontal
or vertical.

$$2^2 = 4 \quad \boxed{} \quad \boxed{} \quad \boxed{}$$

Now identify all possible
rectangles.

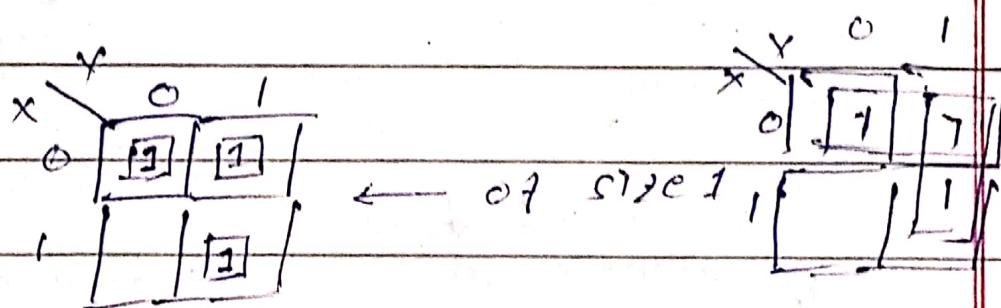

our goal is :-

cover all 1's

with least no of rectangles


Rectangles should be as large as
possible (including maximum no of 1's)

Step 4 :

Remove extra Rectangles.
is there any rectangle
which we can remove and
still cover all Is ??

Step 5 :

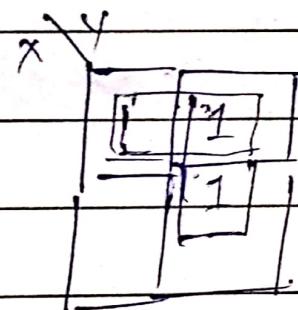write simplified expansion
against each rectangle




label minterms:
while writing
minterms we
wrote:

$$\bar{x} \text{ or } x = 0$$

$$x \text{ " } x = 1$$

Similarly write in K-map

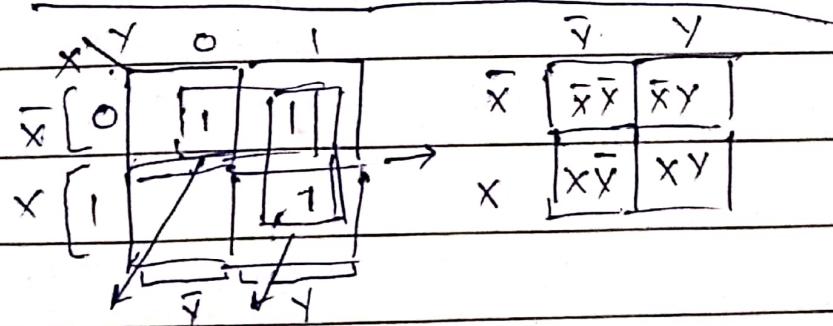

$$F = \bar{x} + y$$

check the sum of min
terms in Rectangle 2 -

$$= \bar{x}\bar{y} + \bar{x}y$$

$$= \bar{x}(y + \bar{y})$$

$$= \bar{x}$$

This is basically what is
common between these two
cells i.e. column in both
cells are different
" " same

→ so simplified equation is

$$\bar{x} + y$$

$$x \quad y \quad | \quad F \quad \bar{x} \quad \bar{x} + y$$

$$0 \quad 0 \quad | \quad 1 \quad 1 \quad 1$$


$$0 \quad 1 \quad | \quad 1 \quad 1 \quad 1$$

$$1 \quad 0 \quad | \quad 0 \quad 0 \quad 0$$

$$1 \quad 1 \quad | \quad 0 \quad 1 \quad 1$$

$$g(A, B) = \sum m(1, 2)$$

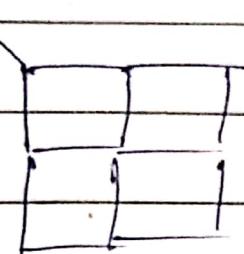notice function variables
are $A \cdot B$



for 2 variable K-map

Rectangle size	no of variable to express it
2	1
1	2

Lecture 9

Three variable maps

$$F(A, B, C) = \Sigma m(0, 1, 2, 3, 4, 5)$$

Notice the variables A, B, C


step 1:

Draw K-map

no of variable = 3

" " mindem = 2^3

" " cell = 2^3 = 8

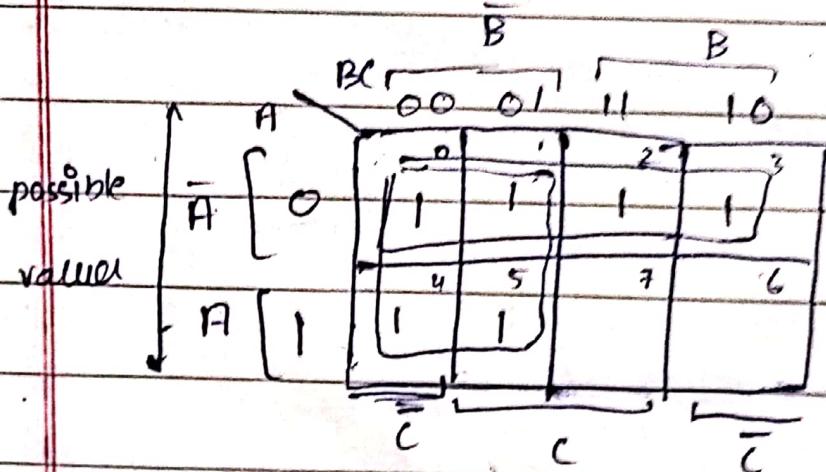

$$F = \bar{A} (1)(1) + \bar{B} (1)(1)$$

$$= \bar{A} + \bar{B}$$

Boof of 07 01 2016:

$$\begin{aligned}
 &= \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}B\bar{C} + \bar{A}B\bar{C} \\
 &= \bar{A}\bar{B}(C + \bar{C}) + \bar{A}B(C + \bar{C}) \\
 &= \bar{A}\bar{B} + \bar{A}B \\
 &= \bar{A}(B + \bar{B}) \Rightarrow \bar{A}
 \end{aligned}$$

$\rightarrow H(A, B; C) = \Sigma m(1, 3, 4, 5, 6)$

		BC	00	01	11	10
		A	0	1	1	0
C	C	0	1	0	1	1
		1	0	1	0	1

$$\bar{A}C + A\bar{B} + A\bar{C}$$

$\rightarrow G_1(A, B, C) = \Sigma m(0, 2, 4, 5, 6)$

		BC	00	01	11	10	why we swap with 2?
		A	0	1	3	12	3 with 2?
C	C	0	1	0	3	12	ans: Because we have to write adjacent cells.
		1	0	1	0	1	

$$\bar{A} + A = 1(B + \bar{B}) \\ = 1(1)\bar{C} = \bar{C}$$

$$AB$$


$$\rightarrow \bar{C} + A\bar{B}$$

→ Four variable map
simplification:

$$F(A, B, C, D) = \sum m(0, 1, 2, 4, 5, 6, 8, 9, 10, 12, 13)$$

no of variables = 4


$$\text{cells} = 2^4 = 16$$

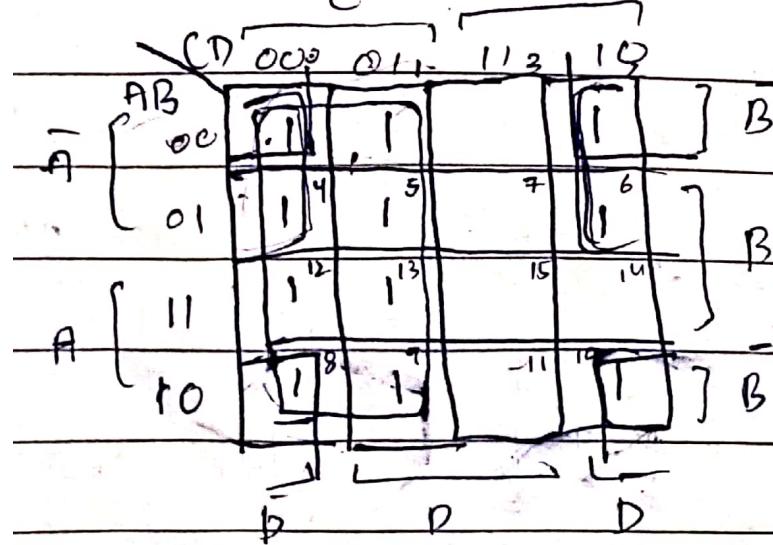

$$= \bar{C} + \bar{A}\bar{D} + \bar{B}\bar{D}$$

Making K-map with the help of equation:
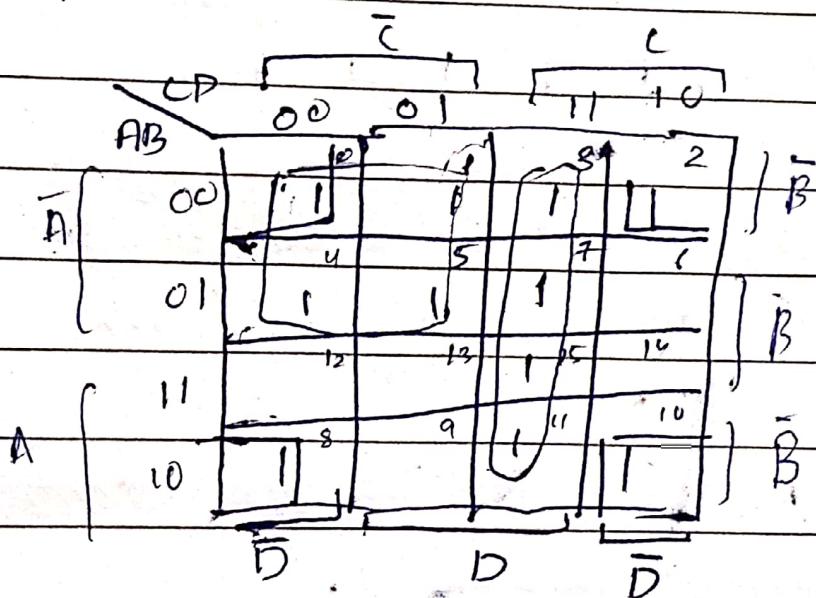
$$G(A, B, C, D) = \bar{A}\bar{C}\bar{D} + \bar{A}D + \bar{B}C + CD + A\bar{B}\bar{D}$$




$$\bar{A}\bar{C} + CD + \bar{B}\bar{D}$$

Prime Implicants

Essential Prime Implicants

non essential prime Implicants

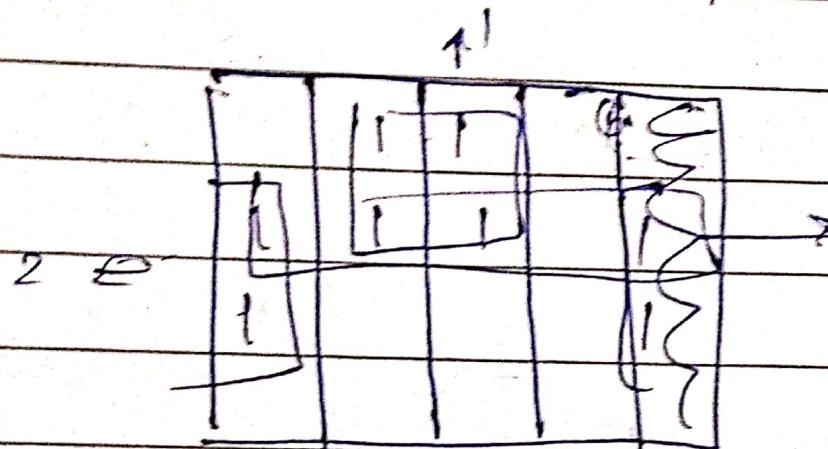


All these 3 rectangles are called prime implicants.

Rectangle ③ is non-essential prime implicant.

Rectangles ① and ② are called essential prime implicants.

Product of sum optimization

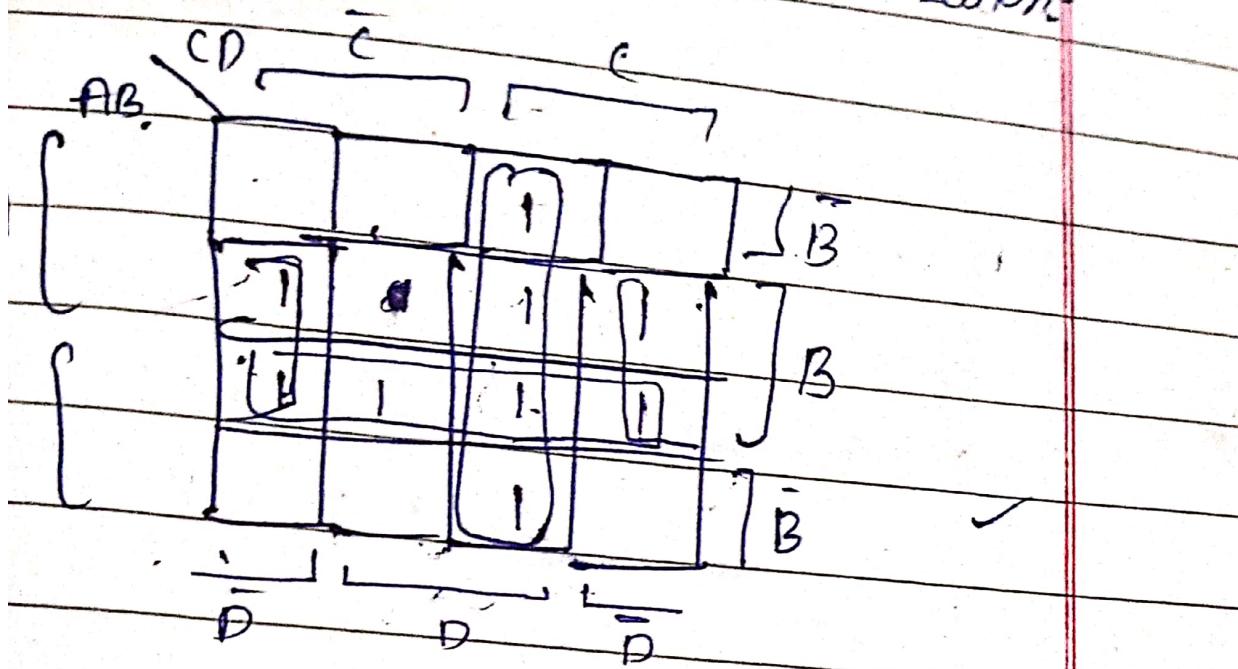

Ans

How :

$$F = (\bar{A} + \bar{B} + D)(\bar{A} + \bar{D})(A + B + \bar{D}) \\ (A + \bar{B} + C + D)$$

Write in product
of sum terms.

Lecture 10

Don't care conditions:-

Suppose we have to design a circuit for a bulb with following requirements.

- Bulb should ON on input 0, 2, 4 and 6.
- Bulb should OFF on input 3 and 5.
- For rest of combinations we don't care about result.

Outputs are said to be unspecified for input combination 1 and 7.

- Functions that have unspecified outputs for some input combinations are called incompletely specified functions.


→ unspecified minterms of function
are called don't care.

Conditions are marked
as X.

- Don't care minterms cannot
be marked as 1 as they.

Other gate types:

Buffers:

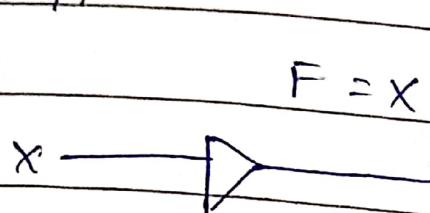

X	F
0	0
1	1

used to amplify an electrical signal if we add negation indicator / bubble at the output it gives inverter symbol.




NAND:

Not AND

X	Y	F
0	0	1
0	1	1
1	0	1

Algebraic equation: $F = \bar{X} \cdot \bar{Y}$

symbol:

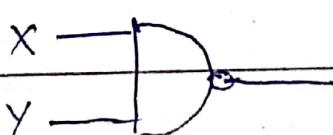

1 1 0

Universal gate:


A gate type that alone can be used to implement all Boolean functions is called universal gate.

① Not logical operation:

$$\text{Equation of NAND: } F = \overline{x \cdot y}$$




If we put $y = x$
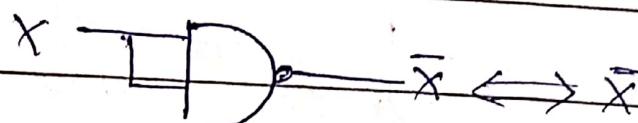
$$F = \overline{x \cdot \overline{x}} = \overline{x} \quad \text{complement operation}$$



② AND logical operation:
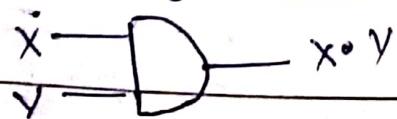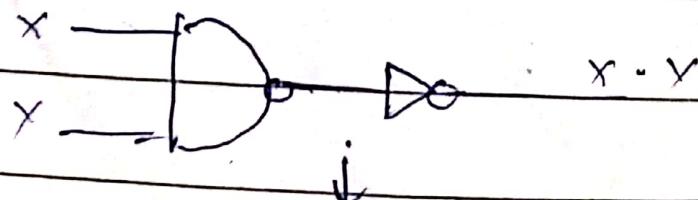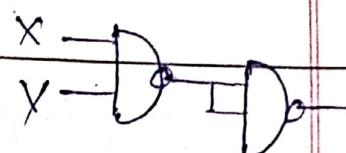
$$F = \overline{\overline{x} \cdot \overline{y}}$$



③ OR logical operation:


OR

Required

$$F = X + Y$$

$$= \overline{\overline{X} + Y}$$

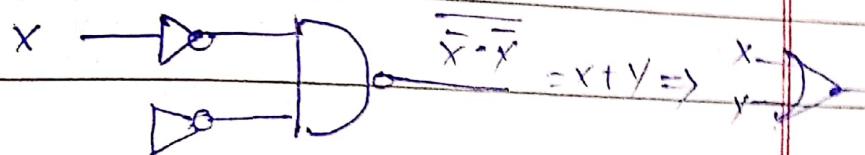
$$= \overline{\overline{X} \cdot \overline{Y}}$$



Since we can perform NOT, NAND and OR logical operation using NAND gate so it is a universal gate.

NOR gate = (NOT OR)

Algebraic equations: $\overline{X+Y}$

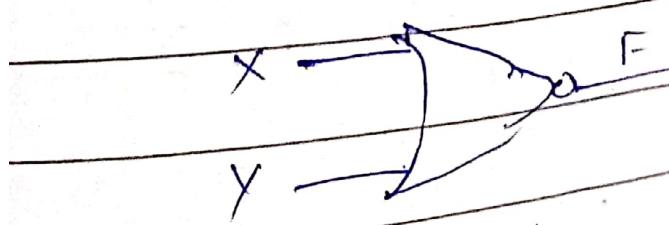

X	Y	F
0	0	1
0	1	0
1	0	0
1	1	0

Can you prove that NOR is a universal gate??

⇒ XOR gate (Exclusive OR):


$$\text{Algebraic eq: } F = X \bar{X} + \bar{X} X$$

$$= X \oplus V$$

\downarrow
XOR operation

Graphic symbol:

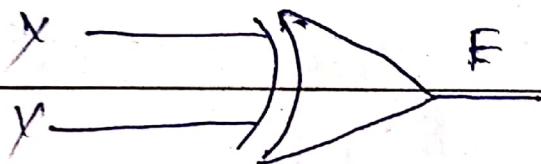- * Give 1 output
- only for odd nos of 1 input.



* If both variables are different, only then $X \oplus Y$ will give result = 1

Available in two input only.

✓ XNOR gate (Exclusive NOR)

$$F = X \bar{X} + \bar{X} \bar{X}$$

$$= \bar{X} \oplus V$$



X	Y	F
0	0	1
0	1	0
1	0	0
1	1	1

xor

M T W T F S

MONDAY

DATE: 1/12/20

XOR • XNOR are used

→ to reduce circuit complexity.

→ " " " cost .

→ " " time required for

to propagate through a circuit .

HW:

Can you prove that

XNOR and XOR are complement

of each other .

XOR

0 0 0

0 1 1

1 0 1

1 1 0

XOR

→ identities apply to XOR operation:

$$x \oplus 0 = x \quad x \oplus 1 = \bar{x}$$

$$x \oplus x = 0 \quad x \oplus \bar{x} = 1$$

$$x \oplus \bar{y} = \bar{x} \oplus y \quad \bar{x} \oplus y = \bar{x} \oplus y$$

Identities can be proved by replacing \oplus operation by its boolean operation.

$$A \oplus B = B \oplus A \text{ (commutative)}$$

$$(A \oplus B) \oplus C = A \oplus (B \oplus C) =$$

$$A \oplus B \oplus C$$

(associative)

M T W T F S

HW CW

DATE: 7/1/20




Technology mapping :- $\text{AND} \rightarrow \text{DoDo}$
 $\text{OR} \rightarrow \text{D} \oplus \text{D}$

Implementation with NAND / NOR:

Implement following optimized
function with NAND gates -


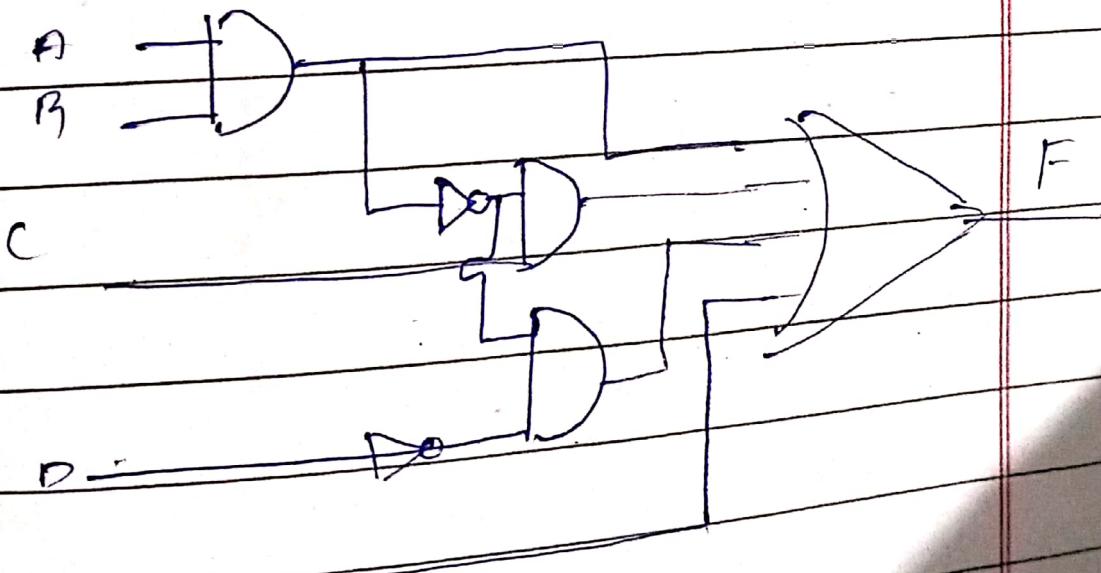
$$F = AB + (\overline{AB})C + (\overline{AB})\overline{D} + E$$



H.W 8

Implement them in
NOT and NOR

→ Parity Generation and checking.

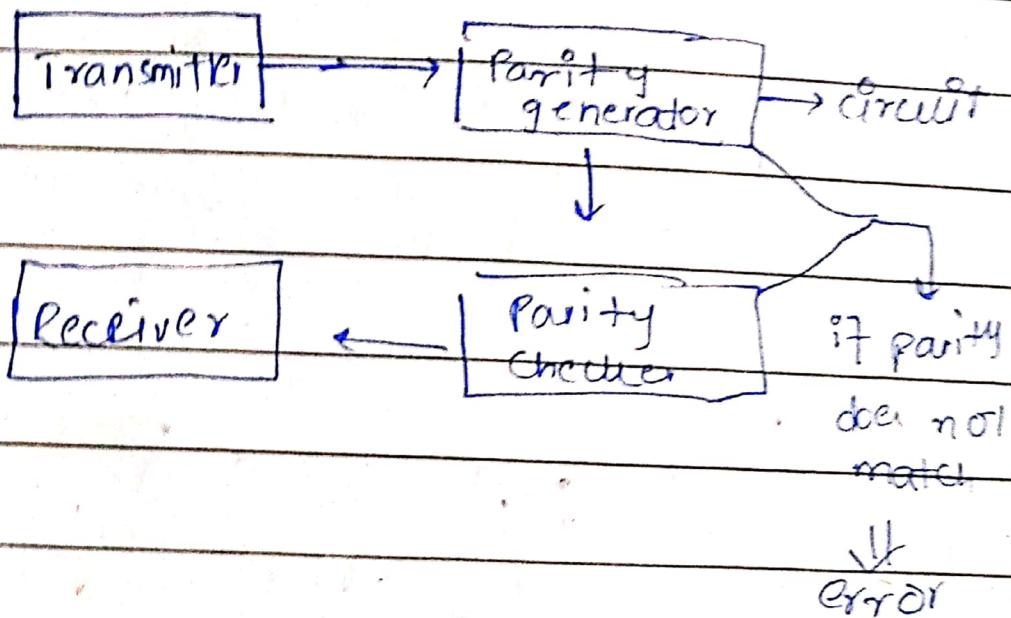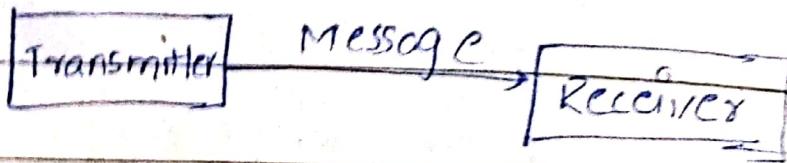

Let's design circuit of parity generator?

Requirement:

We have to transmit

$\frac{4-2}{=}$ $\frac{2}{=}$ $\frac{3}{=}$ bit message with 4th bit

$\frac{2}{=}$ $\frac{1}{=}$ an parity.

First make truth table

2³8


2446 Error parity generator:

DATE: 1/120

Three bit message

X	Y	Z	P
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1
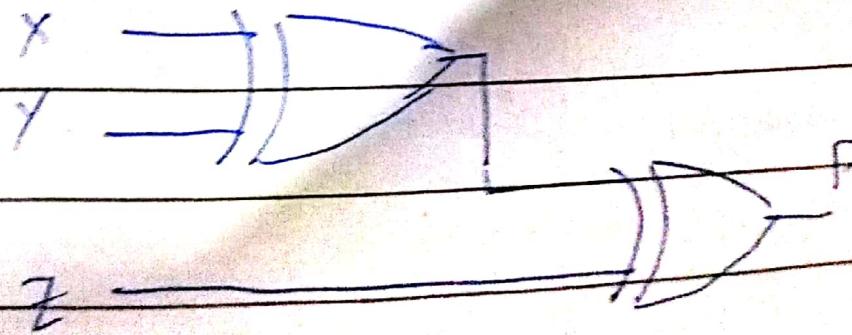
$$F = \bar{x}\bar{y}z + \bar{x}y\bar{z} + xy\bar{z} + xyz$$



$$P = x \oplus y \oplus z$$

→ Parity checker:

Require if parity is odd \rightarrow error (1)
else $\Rightarrow 0$

$$x \cdot x \cdot z = p \quad (c)$$

0 0 0 0 0 $c = 1 \rightarrow \text{error}$

$$0 \quad 0 \quad 0 \quad 1 \quad 1 \quad c = 0 \rightarrow \text{non empty}$$

0 0 1 0 1

0 0 1 1 0

0 1 0 0

0 1 2 3

P = 1

• T T O C

0 | | | |

1 0 0 0 1

1 0 0 1 0

0 1 0 0

1. 2. 3.

Digitized by srujanika@gmail.com

○ ○ ○






101

| | o . |

— — — 0

	0	1	1
	1	1	1
	1	1	1
	1	1	1
	1	1	1

$$C = X \oplus Y \oplus Z \oplus P$$

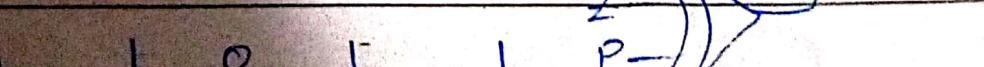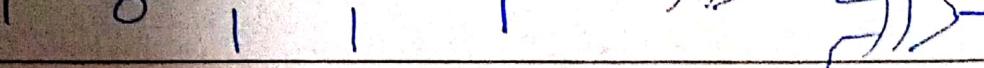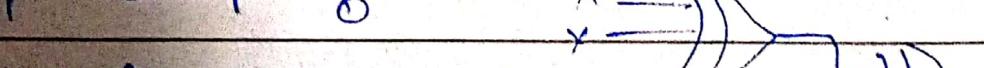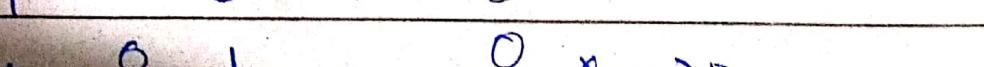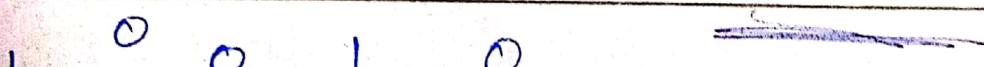

→ Combinational logic design
Procedure:

given a problem statement
we have to design a circuit
example:

design of A B C D - to
excess 3 code converter.

Step 1 :

Specification / Requirements :-

given a decimal digit (in binary
coded decimal) produce
excess - 3 code for that digit

e.g : decimal digit 5

$$5 + 3 = 8 = 1000$$

↓
excess 3 of 5

Express 3 state of decimal digit =

Binary combination
corresponding to decimal
digit plus 3.

Step-2: Formulation:

Derive

* we have to handle
all 2^n combinations

Truth table or initial
equation that define relationship
between circuits.

decimal digit	A	B	C	D	W	X	Y	Z
3 + 0	0	0	0	0	0	0	1	1
3 + 1	0	0	0	1	0	1	0	0
2	0	0	1	0	0	1	0	1
3	0	0	1	1	0	1	1	0
4	0	1	0	0	0	1	1	1
5	0	1	0	1	1	0	0	0
6	0	1	1	0	1	0	0	1
7	0	1	1	1	1	0	1	0
8	1	0	0	0	1	0	1	1
9	1	0	0	1	1	1	0	0
	x	0	1	0	x	x	x	x
		1	0	1	x	x	x	x
		1	1	0	x	x	x	x
		1	1	0	x	x	x	x
		1	1	1	x	x	x	x
		1	1	1	x	x	x	x

For w :

CD 00 01 11 10

AB	00	01	11	10
00				
01			X X X X	
11		X X X X		
10		X X X X		

For x :

CD 00 01 11 10

AB	00	01	11	10
00				
01		1		
11	X X X X			
10	1 X X X			

For y :

CD 00 01 11

AB

AB	00	01	11
00			
01		1	
11	X X X X		
10	1 X X X		

4 bit equality comparators

$$a_3 a_2 a_1 a_0 = b_3 b_2 b_1 b_0$$


$$0000 = 0000 \Rightarrow 1$$

$$0110 \neq 0100 \Rightarrow 0$$




Hierarchical design (divide & conquer)

A_2^c	B_2^c	N_2^c
0	0	0
0	1	1
1	0	1
1	1	0
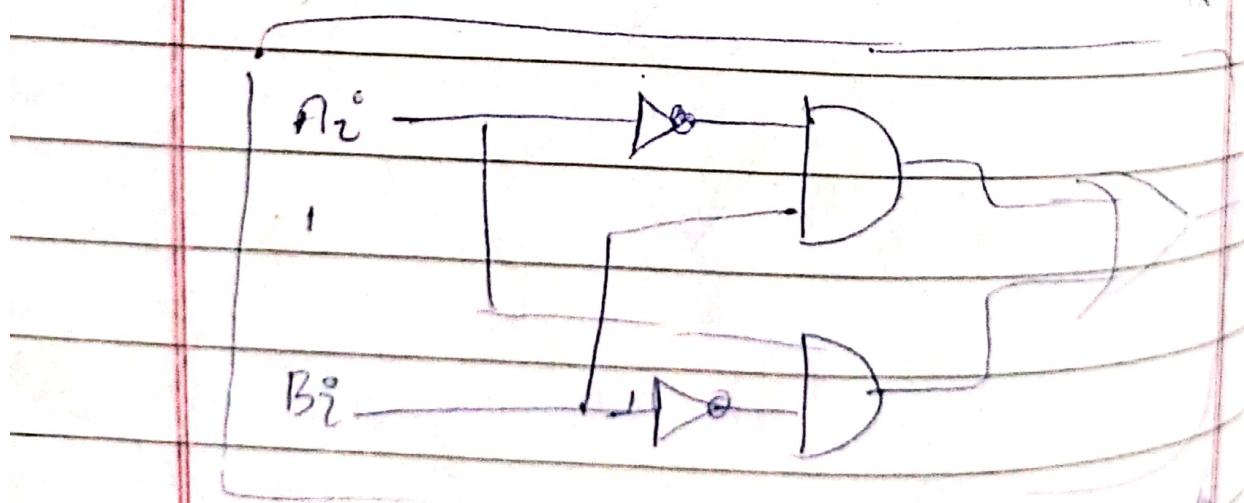
$$\bar{A}_2^c \bar{B}_2^c + N_2^c \bar{B}_2^c$$



1 bit equality comparator

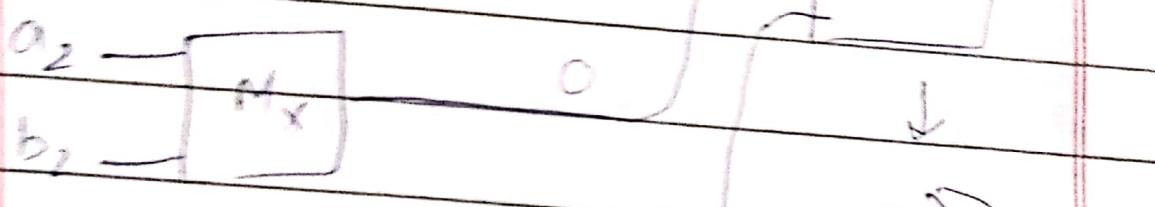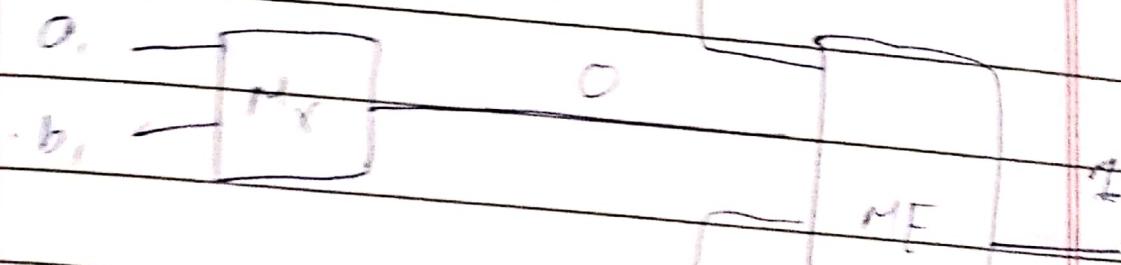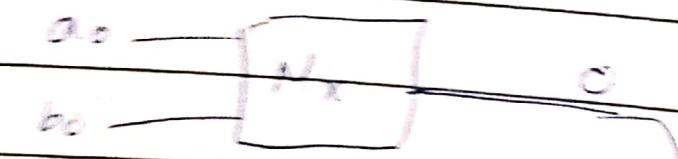

$$N_1 + N_2 + N_3 + N_4$$

Hoklo

99 input odd function